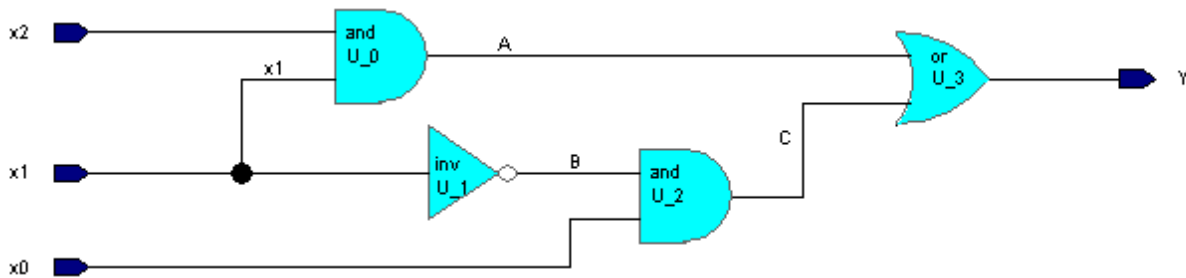


# COMP.CE.200 Digital Design

Fall 2021

## Paper Exercise 3

### Problem 1



Examine the circuit shown above and answer the following questions.

- Determine the output  $y$  equation from the diagram. Use the helper variables A, B, and C.
- What is the critical path assuming each gate has the same **unit delay** regardless of load and gate type?
- Draw the circuit timing when the input sequence is ("111", "111", "111", "101", "101", "101"). The values are given separated by one **unit delay**.  $X = "111"$  is the first input. You can use TimingDraw program and the given wave form or draw by hand using the given template picture.
- How would you fix the problems in the circuit?